




## **Power Electronics Project**

### **Project 1 – PE**

*Sorescu Denis-Valentin, 1.2*

*Toth Razvan-Catalin, 1.2*

*Slejiuc Robert-Andrei, 1.2*

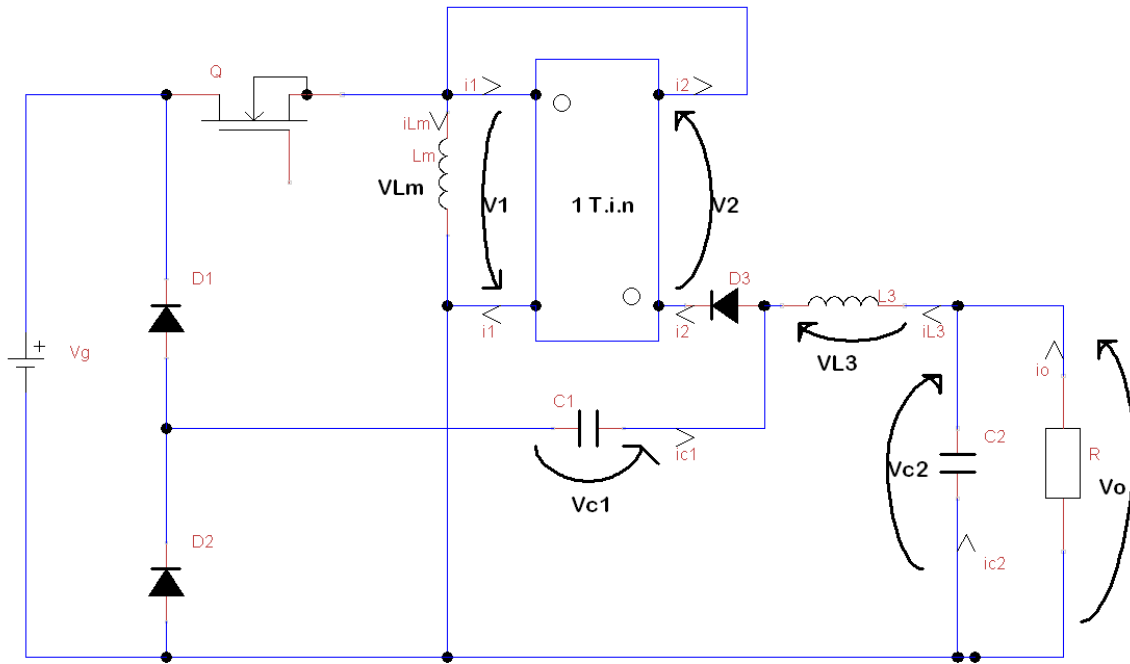

**Design values known:**

- $Vg(\min) \div Vg(\max)$
- $Vo, \Delta Vo, f_s$
- $Po(\min) \div Po(\max)$

Transformer equations:

$$\left\{ \begin{array}{l} v_1 = \frac{v_2}{n} \\ i_1 + n i_2 = 0, \end{array} \right.$$

In which we derive:  $n = \frac{N_2}{N_1}$ ;

**1. Justify why the direction of capacitor voltages and inductor currents have been chosen as such, and how do they result positive.**

$$i_{L_3} = i_{D_3} + i_{C_1} ;$$

$$\text{In DC we know that : } i_{L_3} = i_{D_3} > 0;$$

$$v_{C_2} = -v_{L_m} - v_2 + v_{D_3} - v_{L_3} ;$$

$$\text{For DC: } V_{L_m} = V_{L_3} = 0 \Rightarrow V_2 = 0 \Rightarrow V_{C_2} = V_{D_3} > 0 ;$$

$$v_{C_1} = v_{D_2} + v_{C_2} + v_{L_3} , \text{ so we can see that } V_{C_1} = V_{D_2} + V_{C_2} > 0 ;$$

$$i_{L_m} = i_Q - i_1 , \text{ in which we derive that } i_1 = -ni_2 , \text{ but } i_2 = i_{D_3} \Rightarrow \\ \Rightarrow i_{L_m} = i_Q + ni_{D_3} \Rightarrow i_{L_m} = i_Q + ni_{D_3} > 0 ;$$

**2. Justification for the conduction state of the diodes.**

We can assume that in the first state(ON state), Q and  $D_1$  are conducting, and  $D_2$  with  $D_3$  are off.

ON state: -Q &  $D_1$ (conducting);

- $D_2$ & $D_3$ (off);


$$i_{D_3} = 0 \Rightarrow i_2 = 0 \Rightarrow i_1 = -ni_2 = 0;$$

$$i_Q = i_{L_m} + i_1 - i_2 = i_{L_m} > 0;$$

$$i_{D_1} = i_{D_2} - i_{C_1} = -i_{C_1} = -(-i_{L_3}) = i_{L_3} > 0;$$

$$v_{D_2} = V_g > 0;$$
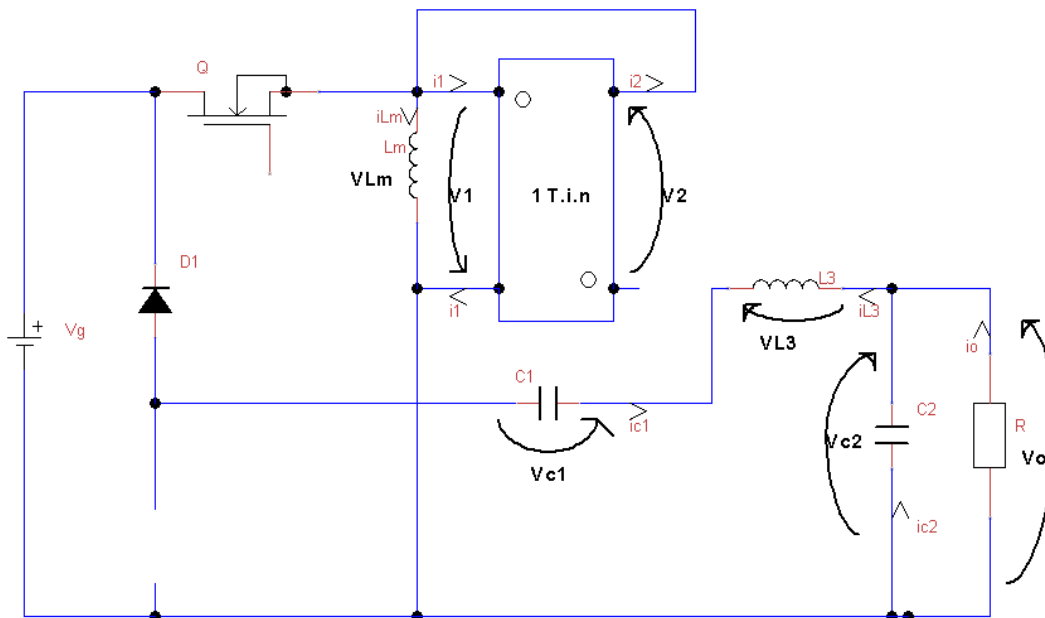
$$v_{D_3} = v_2 + v_{C_1} = v_{C_1} + v_{L_m} = v_{C_1} + nV_g > 0;$$



Equations resulted:


$$v_{L3ON} = v_{C1} - v_{C2} - V_g;$$

$$v_{LmON} = V_g;$$

$$i_{C1ON} = -i_{L3};$$

$$i_{C2ON} = i_{L3} - \frac{v_{C2}}{R};$$

OFF state:

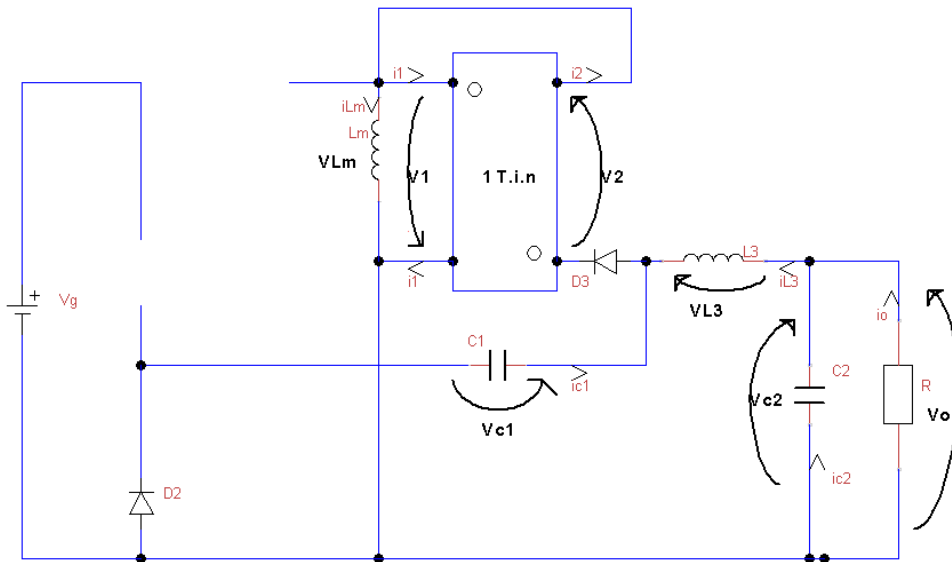

Equations resulted:

$$v_{L3OFF} = -v_{C2} + v_{C1};$$

$$v_{LmOFF} = -\frac{v_{C1}}{n+1};$$


$$i_{C1OFF} = \frac{i_{Lm}}{n+1} - i_{L3};$$

$$i_{C2OFF} = i_{L3} - \frac{v_{C2}}{R};$$

Ideal static conversion ratio – final formula :

$$M_{IDEAL} = \frac{D}{1-D} (n + D);$$

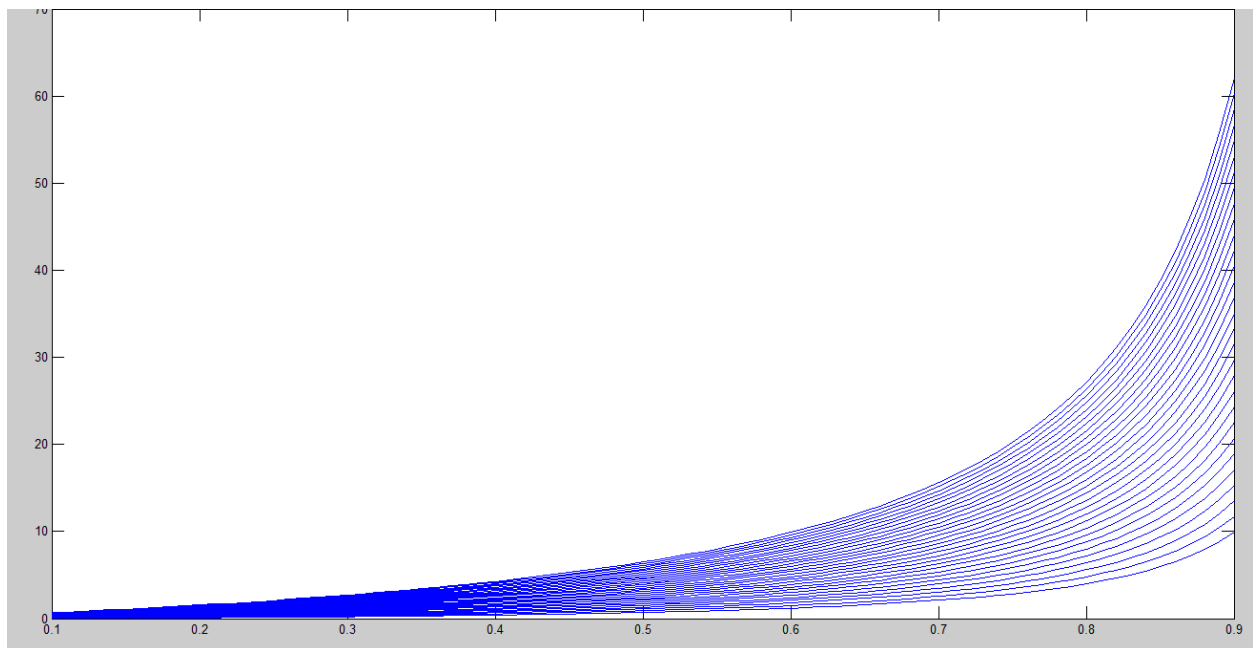
***4. Static conversion ratio representation against the duty cycle with turns ratio as a parameter.***



From the resulted graph, we can see that we have a buck-boost converter type.

At low duty cycles (under 0.25), we have a static conversion ratio which is underlimited, and as the duty cycle rises, the converter continues to ramp up in power.

## 5. Waveforms

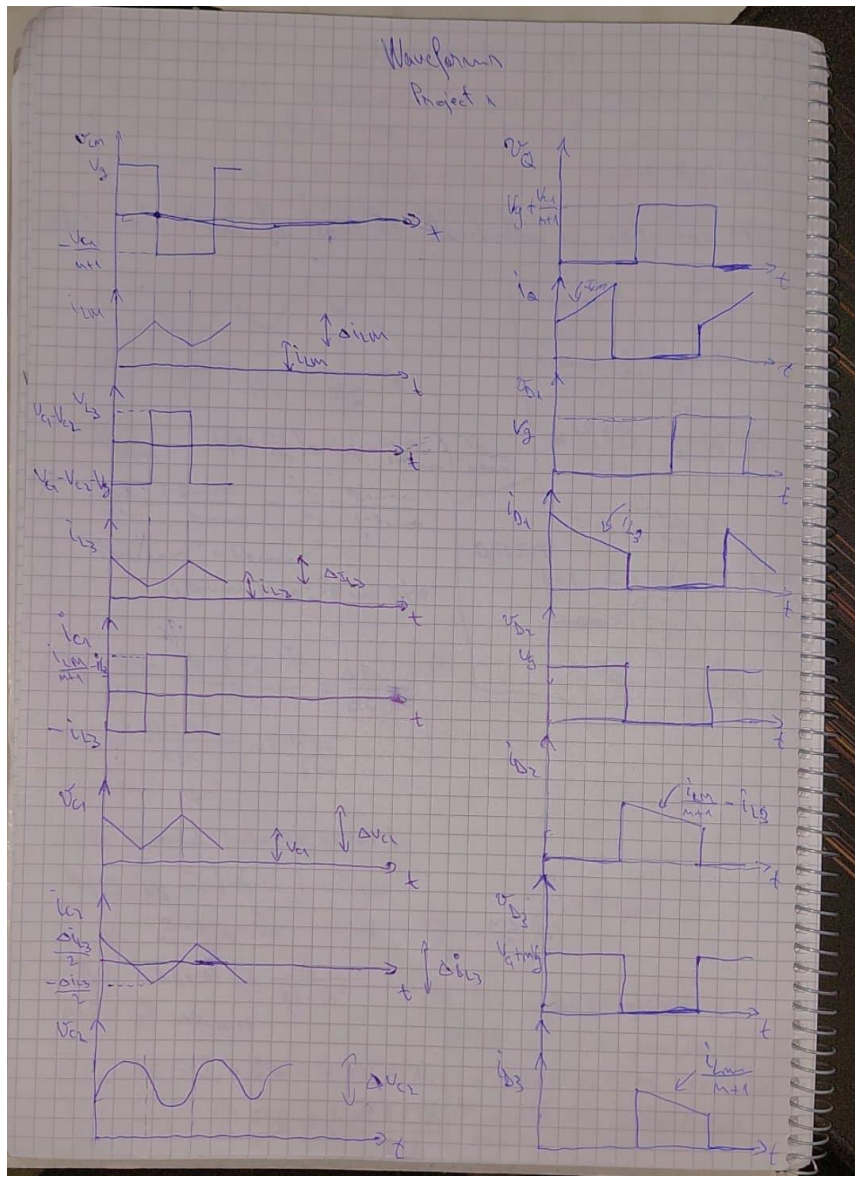

**6. Ripple calculation in terms of dc supply voltage, dc output voltage, output power converter and switching freq.**

$$v_{L_{mON}} = L_m \frac{\Delta i_{L_m}}{DT_s} \Rightarrow \Delta i_{L_m} = \frac{v_{L_{mON}} DT_s}{L_m} \Rightarrow \Delta i_{L_m} = \frac{DV_g}{L_m f_s};$$

$$v_{L_{3OFF}} = L_3 \frac{\Delta i_{L_3}}{(1-D)T_s} \Rightarrow \Delta i_{L_3} = \frac{(1-D)(v_{C_1} - v_{C_2})}{L_3 f_s} \Rightarrow \Delta i_{L_3} = \frac{D(1-D)V_g}{L_3 f_s};$$

$$|i_{C_{1ON}}| = C_1 \frac{\Delta v_{C_1}}{DT_s} \Rightarrow \Delta v_{C_1} = \frac{i_{L_3} D}{C_1 f_s} \Rightarrow \Delta v_{C_1} = \frac{D^2(n+D)V_g}{(1-D)R C_1 f_s};$$

For the formula of  $\Delta v_{C_2}$  we need to consider load for  $\Delta v_{C_1} = \frac{\Delta Q}{C_2}$ , where we deduce that

$$\Delta Q = \frac{1}{2} \frac{T_s}{2} \frac{\Delta i_{L_3}}{2} \Rightarrow \Delta v_{C_2} = \frac{D(1-D)V_g}{8 C_2 L_3 f_s^2};$$



**7. Semiconductor voltage and current stresses formulas resulted based on  $V_o$ ,  $P_o$ ,  $V_g$ , and  $n$ .**

We get :  $\frac{D}{1-D}(n + D) = \frac{V_o}{V_g} \Rightarrow D = f(V_o, V_g, n);$

$$P_o = \frac{V_o^2}{R} \Rightarrow R = \frac{V_o^2}{P_o};$$

Approximate for calculus ( $v_{C_1} \sim V_{C_1}$ ,  $v_{C_2} \sim V_{C_2}$ ):

$$V_{Q_{mean}} = (1 - D) \left( V_g + \frac{V_{C_1}}{n+1} \right);$$

RMS values:

$$V_{D_1_{mean}} = (1 - D)V_g;$$

$$1 - D \rightarrow \sqrt{1 - D};$$

$$V_{D_2_{mean}} = DV_g;$$

$$D \rightarrow \sqrt{D};$$

$$V_{D_3_{mean}} = D(V_{C_1} + nV_g);$$

Identical otherwise.

### **8. Conditions for CCM operations, canonical form.**

For D1;

$$i_{D_1} \geq 0 \leftrightarrow i_{D_{1_{min}}} \geq 0 \Rightarrow i_{L_3} - \frac{\Delta i_{L_3}}{2} \geq 0;$$

$$\begin{aligned} \frac{D(D+n)V_g}{1-D} \frac{1}{R} &\geq \frac{D(1-D)V_g}{2L_3 f_s} \Rightarrow \frac{2L_3 f_s}{R} \geq \frac{D(1-D)^2}{D(D+n)} \Rightarrow \frac{2L_3 f_s}{R} \\ &\geq \frac{(1-D)^2}{(D+n)}; \end{aligned}$$

For D2;

$$i_{D_2} \geq 0 \leftrightarrow i_{D_{2_{min}}} \geq 0 \Rightarrow \frac{\Delta i_{L_m}}{n+1} - i_{L_3} - \frac{\Delta i_{L_m}}{2(n+1)} + \frac{\Delta i_{L_3}}{2} \geq 0;$$

$$\frac{DV_g(D+n)}{R(D-1)} - \frac{DV_g}{2L_m f_s(n+1)} - \frac{DV_g(D-1)}{2L_3 f_s} + \frac{DV_g(D+n)}{R(D-1)^2};$$

For D3;

$$i_{D_3} \geq 0 \leftrightarrow i_{D_{3_{min}}} \geq 0 \Rightarrow \frac{i_{L_m}}{n+1} - \frac{\Delta i_{L_m}}{2(n+1)} \geq 0;$$

$$\frac{D(D+n)V_g}{R(1-D)^2} \geq \frac{DV_g}{2L_m f_s(n+1)} \Rightarrow \frac{2L_m f_s}{R} \geq \frac{(1-D)^2}{(n+1)(D+n)};$$

**9. Initial relationships for inductors and capacitor design, with Matlab final numerical results.**

Vg\_min=15; Vg\_max=18; Vo=25; Po\_min=25; Po\_max=50; dvo=0.25; fs=100e3;

```
L1 =  
    1.1718e-04  
  
L2 =  
    3.0612e-05  
  
L3 =  
    1.7708e-04  
  
C1 =  
    1.6580e-05  
  
C2 =  
    1.2500e-06
```

 >>

Choose  $D_{max}$  in case of  $V_{min}$  and get rid of  $n$ ; Calculate  $D_{min}$  for  $V_{max}$ ;  
 $D_{min} < D < D_{max}$ ;

### **10. Power stage simulation for ideal converter(Table).**

V<sub>g</sub>=18; R=25; D=0.5637; n=0.5111; L<sub>3</sub>=180e-6; C<sub>1</sub>=16.5e-6; C<sub>2</sub>=1.25e-6; L<sub>m</sub>=120e-6; f<sub>s</sub>=100e3;

Program used	MATLAB	CASPOC
I <sub>Q</sub> _mean	1.9520	1.960
I <sub>Q</sub> _rms	2.5999	2.613
I <sub>D1</sub> _mean	0.5636	0.5657
I <sub>D1</sub> _rms	0.7507	0.7543
I <sub>D2</sub> _mean	0.5636	0.5634
I <sub>D2</sub> _rms	0.8533	0.8681
I <sub>D3</sub> _mean	0.9998	0.9996
I <sub>D3</sub> _rms	1.5137	1.519
V <sub>Q</sub> _mean	18	18
V <sub>DS</sub>	41.256	
V <sub>D3</sub>	44,342	44,34V
V <sub>out</sub> _mean	25	25.016
V <sub>out</sub> _rms	25	25.010

### **11. Main parameters of the devices, semiconductors and the loss parameters.**

**Transistor:** N-MOSFET; unipolar; 500V; 4A; 29,2W; TO220FP;

**The 3 Diodes:** rectifier Schottky; THT; 60V; 2A; DO15; Package from : Ammo Pack;

**Condensator C1:** electrolytic; reduced impedance; THT; 18uF; 63VDC;

**Condensator C2 out:** electrolytic; THT; 1,5uF; 50VDC; Ø4x7mm; Pitch: 1,5mm;

*The diodes have been chosen uniformly as the same type for them to have consistent diode forward turn-on time ( commutation).*

## **12. $D_{max}$ and $D_{min}$ resulted from Matlab.**


$$D_{max} = 0.6414;$$

$$D_{min} = 0.6008;$$
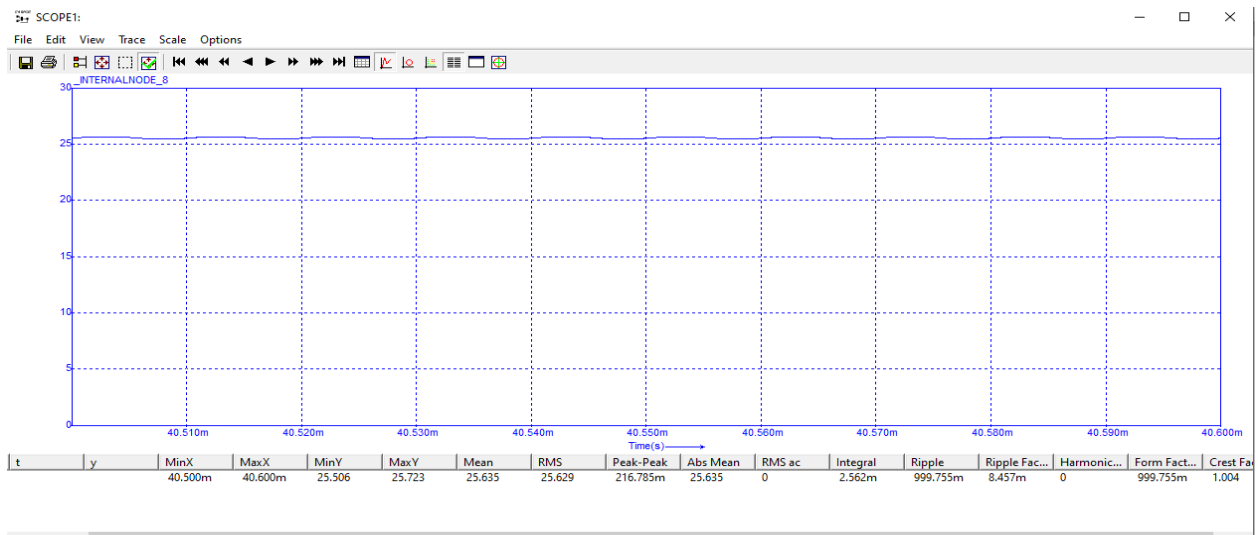
## **13. Operating point arbitrarily chosen and Output Ripple Voltage**

We chose the operating point  $V_{max} = 18V$ , for which it corresponds to the following minimum duty cycle chosen at point 10  $D_{min} = 0.6008$ ;

Output voltage ripples are in the allowed limits, as seen in the photo provided (Peak-Peak for reference value).



$$Ripple_{V_{out}} = 216.785mV;$$